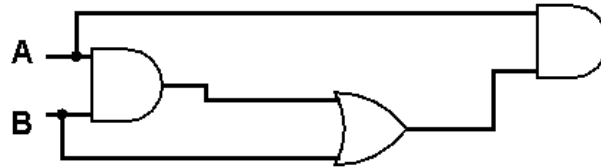



### Review Questions 9

For the following logic diagrams, determine the final output, then reduce the output expression using the reference table and draw its equivalent, verify using the truth table


1.




2.

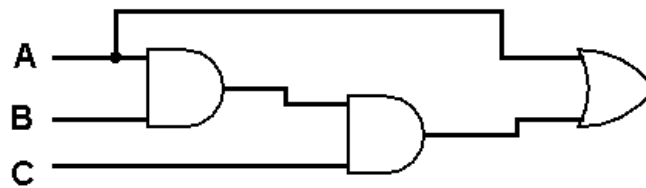

3.

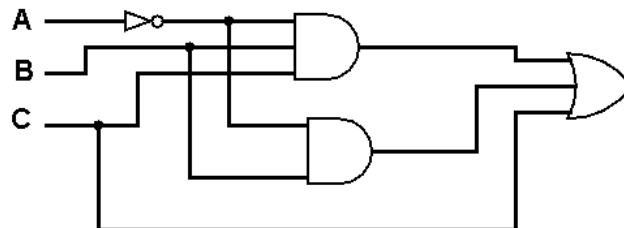

4.

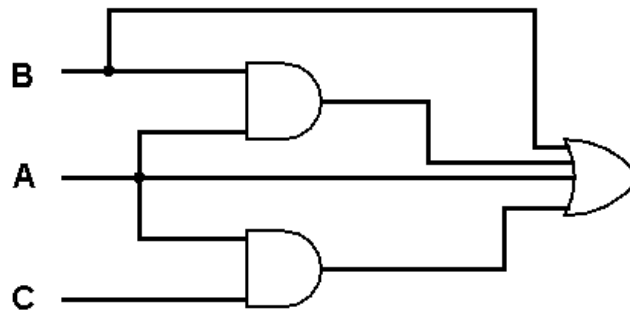

**Answers:**

1.  $A(AB+B)$  reduces to  $AB$
2.  $ABC+A$  reduces to  $A$
3.  $\overline{A}BC+\overline{A}B+C$  reduces to  $\overline{A}B+C$
4.  $AB+AC+B+A$  reduces to  $A+B$