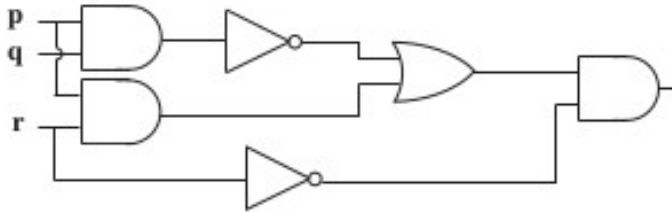



Review Questions for Test #2

For the following logic circuits, determine the final output, reduce the final output expression algebraically to a simpler form, draw the simplified logic diagram, verify the 2 algebraic expressions are equivalent to one another using the truth table.


1.



2.

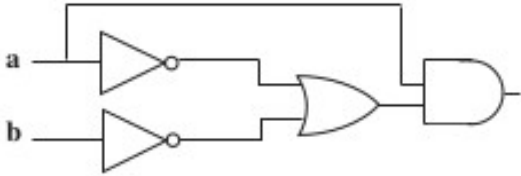

3.

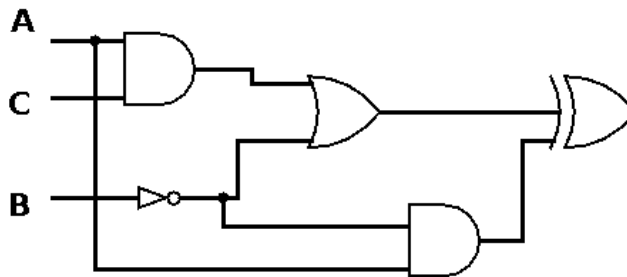

Use De Morgan's theorem and the reference table to simplify the following Boolean expressions

4. $\overline{(\overline{AB})(\overline{C+D})}$

5. $\overline{A+B(C+\overline{A}B)}$

6. $\overline{(\overline{A}B)(\overline{C}B+A)}$

7. $\overline{\overline{A}+B(C+\overline{D})+FG}$

Simplify the following Boolean expressions using the algebraic properties and reference table

8. $AB + A(B + C) + B(B + C)$

9. $\overline{C}(D + AB) + \overline{A}B(CD + A) + A(BC + A)$

10. $(B + A)(AC + B) + BC(\overline{A} + BC) + AB(\overline{C} + B)$

11. $(PQ) \oplus (P + RQ)$

Answers to Test #2 Review Questions

1. $(\overline{P} + \overline{Q})\overline{R} = \overline{P}\overline{R} + \overline{Q}\overline{R}$

2. $A\overline{B}$

3. $(AC + \overline{B}) \oplus (A\overline{B})$ reduces to $ABC + \overline{A}\overline{B}$

4. $AB + C + D$

5. $\overline{A}\overline{B}$

6. $A + \overline{A}C + \overline{B} = A + \overline{B} + C$


7. $A[\overline{B} + \overline{C}D][\overline{F} + \overline{G}] = A(\overline{B} + \overline{C})(D + \overline{B})(\overline{F} + \overline{G})$

8. $B + AC$

9. $A + \overline{A}BCD + \overline{C}D = A + (B + \overline{C})D$

10. $AC + B$

11. $\overline{P}RQ + \overline{Q}P$

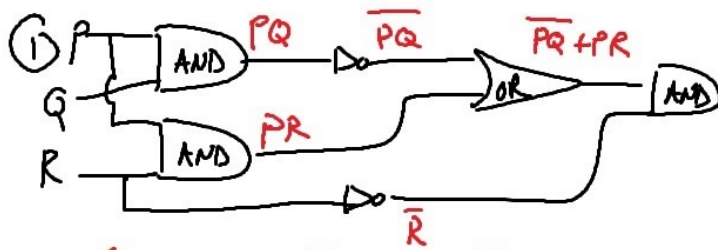


$$I_5: (PQ + PR)\bar{R} = \bar{R}(\bar{P} + \bar{Q})?$$


$$\bar{P}\bar{R} + \bar{Q}\bar{R} + P\bar{R}\bar{R}$$

$$\bar{P}\bar{R} + \bar{Q}\bar{R}$$

$$\bar{R}(\bar{P} + \bar{Q})$$

P	Q	R	\bar{P}	\bar{Q}	\bar{R}	PQ	$\bar{P}\bar{Q}$	PR	$\bar{P}\bar{Q} + PR$	$(\bar{P}\bar{Q} + PR)\bar{R}$	$\bar{P} + \bar{Q}$	$(\bar{P} + \bar{Q})\bar{R}$
0	0	0	1	1	1	0	1	0	1	1	1	1
0	0	1	1	1	0	0	1	0	1	0	1	0
0	1	0	1	0	1	0	0	0	0	0	1	0
0	1	1	1	0	0	0	0	0	0	0	1	0
1	0	0	0	1	1	0	1	0	1	1	0	0
1	0	1	0	1	0	0	1	1	1	0	0	0
1	1	0	0	0	1	1	0	0	1	1	0	0
1	1	1	0	0	0	1	0	1	1	0	0	0

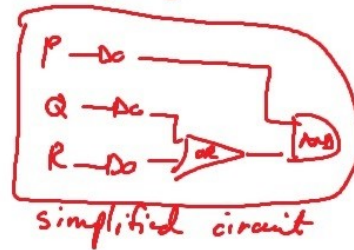

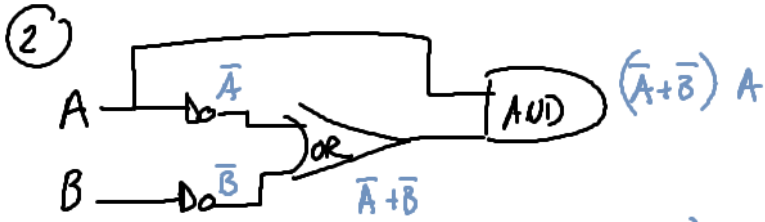

Is $A(\overline{A} + \overline{B}) = A\overline{B}$?

A	B	\overline{A}	\overline{B}	$\overline{A} + \overline{B}$	$A(\overline{A} + \overline{B})$	$A\overline{B}$
0	0	1	1	1	0	0
0	1	1	0	1	0	0
1	0	0	1	1	1	1
1	1	0	0	0	0	0

correct
 match \therefore


$A(\overline{A} + \overline{B})$ \downarrow 123


$A\overline{A} + A\overline{B}$

\downarrow &


$0 + A\overline{B}$

$A\overline{B}$

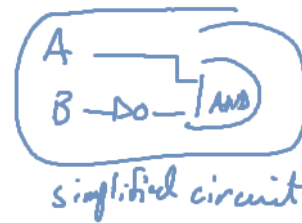

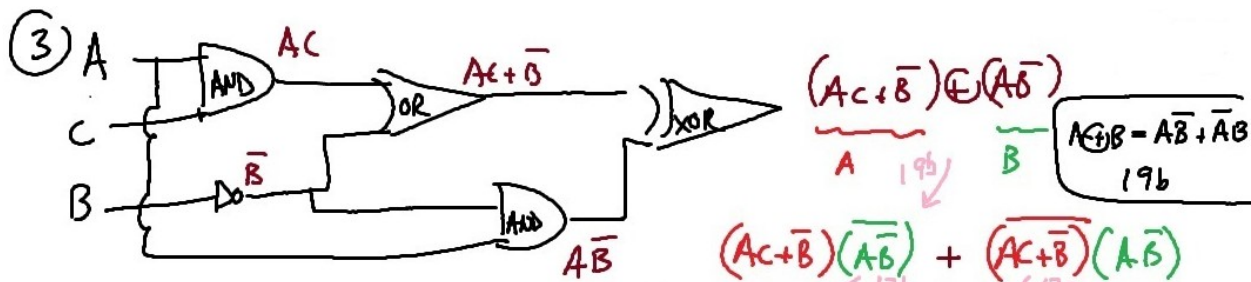
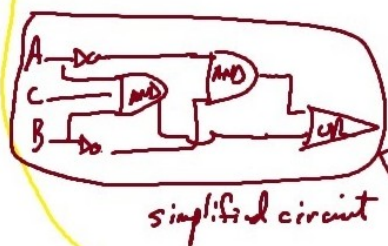
$$I_5 (A + \bar{B}) \oplus (\bar{A} \bar{B}) = ABC + \bar{A} \bar{B} ?$$



[illegible]

correct

match

A	B	C	\bar{A}	\bar{B}	AC	$A+\bar{B}$	$A\bar{B}$	$AC+\bar{B} \oplus A\bar{B}$	ABC	$\bar{A}\bar{B}$	$A\bar{B} + \bar{A}\bar{B}$
0	0	0	1	1	0	1	0	1	0	1	1
0	0	1	1	1	0	1	0	1	0	1	1
0	1	0	1	0	0	0	0	0	0	0	0
0	1	1	1	0	0	0	0	0	0	0	0
1	0	0	0	1	0	1	1	1	0	0	0
1	0	1	0	1	0	1	1	1	0	0	0
1	1	0	0	0	0	0	0	0	0	0	0
1	1	1	0	0	1	0	0	0	0	0	0

$$\begin{aligned}
 & \textcircled{4} \quad \overline{(\overline{AB})(\overline{C+D})} \\
 & \quad \overline{(\overline{AB}) + (\overline{C+D})} \quad \text{13b} \\
 & \quad \downarrow \text{9a} \quad \downarrow \\
 & \quad \boxed{AB + C + D}
 \end{aligned}$$

$$\begin{aligned}
 & \textcircled{5} \quad \overline{A + B(C + \overline{AB})} \\
 & \quad \overline{A + BC + \overline{AB}B} \quad \text{12a} \\
 & \quad \overline{A + BC + \overline{AB}} \quad \text{6a} \\
 & \quad \text{13b} \quad \overline{(\overline{A})(\overline{BC})(\overline{AB})} \\
 & \quad \quad \downarrow \text{13a} \quad \downarrow \\
 & \quad \overline{A}(\overline{B} + \overline{C})(\overline{A} + \overline{B}) \\
 & \quad \quad \downarrow \text{9a} \\
 & \quad \overline{A}(\overline{B} + \overline{C})(A + \overline{B}) \\
 & \quad \quad \downarrow \text{12a} \\
 & \quad \overline{(\overline{A}\overline{B} + \overline{A}\overline{C})(A + \overline{B})} \quad \text{FOIL} \\
 & \quad \quad \overline{(\overline{A}\overline{A}\overline{B} + \overline{A}\overline{B}\overline{B} + \overline{A}\overline{A}\overline{C} + \overline{A}\overline{B}\overline{C})} \\
 & \quad \quad \downarrow \text{Fa} \quad \downarrow \text{Fa} \\
 & \quad \quad \overline{(\overline{0}\overline{B} + \overline{A}\overline{B} + \overline{0}\overline{C} + \overline{A}\overline{B}\overline{C})} \\
 & \quad \quad \overline{A}\overline{B} + \overline{A}\overline{B}\overline{C} \\
 & \quad \quad \overline{A}\overline{B}(1 + \overline{C}) \quad \text{factoring} \\
 & \quad \quad \downarrow \text{SL} \\
 & \quad \quad \overline{A}\overline{B}(1) \rightarrow \boxed{\overline{A}\overline{B}}
 \end{aligned}$$

$$\textcircled{6} \overline{(\bar{A}B)(\bar{C}B+A)}$$

$$\bar{A}B\bar{B}\bar{C} + \bar{A}AB$$

$$\bar{A}B\bar{C} + \cancel{0B}$$

$$\overline{\bar{A}B\bar{C}}$$

$$\overline{\bar{A}} + \overline{\bar{B}} + \overline{\bar{C}}$$

$$A + B + C$$

$$\textcircled{7} \quad \overline{A + B(C + \overline{D}) + FG}$$

$$\overline{A + BC + B\overline{D} + FG}$$

$$(\overline{A})(\overline{BC})(\overline{B\overline{D}})(\overline{FG})$$

$$(A)(\overline{B+C})(\overline{B+\overline{D}})(\overline{F+G})$$

$$A(\overline{B+C})(\overline{B+D})(\overline{F+G})$$

$$\text{FOIL } \downarrow (\overline{B+C})(\overline{B+D})(\overline{F+G})A$$

$$(\overline{B}\overline{B} + \overline{B}D + \overline{B}\overline{C} + \overline{C}D)(\overline{F+G})A$$

$$(\overline{B} + \overline{B}D + \overline{B}\overline{C} + \overline{C}D)(\overline{F+G})A$$

$$\text{factoring } \downarrow \{ \overline{B}[1 + D + \overline{C}] + \overline{C}D \} (\overline{F+G})A$$

$$\{ \overline{B}[1] + \overline{C}D \} (\overline{F+G})A \rightarrow \overline{B} + \overline{C}D \} (\overline{F+G})A$$

$$(8) \quad AB + A(B+c) + B(B+c)$$

$$AB + AB + AC + BB + BC$$

$$\underbrace{AB}_{6b} + AC + \underbrace{B}_{6a} + BC$$

$$AC + AB + B + BC$$

$$AC + (A + 1 + c)B$$

$$\downarrow \text{factoring}$$

$$\underbrace{AC}_{5b} + (1)B$$

$$\boxed{AC + B}$$

$$\begin{aligned}
 & \textcircled{9} \quad \overline{C}(D+AB) + \overline{A}B(CD+A) + A(BC+A) \\
 & \quad \downarrow 12a \quad \downarrow 12a \quad \downarrow 12a \quad \downarrow 6a \\
 & (\overline{C}D + ABC) + (\overline{A}BCD + A\overline{A}B) + (ABC + AA) \\
 & \quad \downarrow 8a \quad \downarrow 6a \\
 & \overline{C}D + ABC + \overline{A}BCD + \cancel{0B} + ABC + A \\
 & \overline{C}D + \overline{A}BCD + ABC + ABC + A \\
 & \overline{C}D + \overline{A}BCD + (BC + BC + 1)A \quad \downarrow \text{factoring} \\
 & \quad \downarrow 5b \\
 & \overline{C}D + \overline{A}BCD + (1)A \\
 & \overline{C}D + \overline{A}BCD + A \\
 & \quad \downarrow \text{absorption via 12b} \\
 & \overline{C}D + (\overline{A}+A)(A+BCD) \\
 & \quad \downarrow 8b \\
 & \overline{C}D + (1)(A+BCD) \\
 & A + \overline{C}D + BCD \quad \downarrow \text{factoring} \\
 & A + (\overline{C} + BC)D \\
 & \quad \downarrow \text{absorption via 12b} \\
 & A + [(\overline{C}+B)(\overline{C}+C)]D \\
 & \quad \downarrow 8b \\
 & A + [(\overline{C}+B)(1)]D \\
 & \boxed{A + (\overline{C}+B)D}
 \end{aligned}$$

$A+BC = (A+B)(A+C)$
12b

$$\begin{aligned}
 & \textcircled{10} (B+A)(Ac+B) + BC(\bar{A}+BC) + AB(\bar{C}+B) \\
 & \quad \text{FOIL} \quad \quad \quad \downarrow \text{12a} \quad \quad \quad \downarrow \text{12a} \\
 & (ABC + BB + AAC + AB) + (\bar{A}BC + BBCC) + (AB\bar{C} + ABB) \\
 & ABC + B + AC + AB + \bar{A}BC + BC + AB\bar{C} + AB \\
 & ABC + B + AB + \bar{A}BC + BC + AB\bar{C} + AB + AC \\
 & \downarrow \text{factoring} \\
 & B(AC + 1 + A + \bar{A}C + C + A\bar{C} + A) + AC \\
 & \quad \quad \quad \downarrow \text{5b} \\
 & B(1) + AC \longrightarrow \boxed{B+AC}
 \end{aligned}$$

$$(11) \quad \underbrace{PQ}_A + \underbrace{(P + RQ)}_B \quad \downarrow 19b$$

$$A \oplus B = A \bar{B} + \bar{A} B$$

19b

$$(PQ)(\overline{P + RQ}) + (\overline{PQ})(P + RQ)$$

$$(PQ)(\overline{P + RQ}) + (\overline{PQ})(P + RQ) \quad \downarrow 13a \quad \downarrow 13b$$

$$(PQ)(\overline{P + RQ}) + (\overline{PQ})(P + RQ) \quad \downarrow 13b \quad \downarrow \text{FOIL}$$

$$PQ(\overline{P + RQ}) + (\overline{PQ})(P + RQ) \quad \downarrow 12a \quad \downarrow 8a \quad \downarrow 8a$$

$$P\bar{P}\bar{R}Q + P\bar{P}Q\bar{Q} + 0 + \bar{P}RQ + P\bar{Q} + \cancel{RQ}$$

$$\cancel{0 \cdot \bar{R}Q} + \cancel{0 \cdot Q} +$$

$$\boxed{\bar{P}RQ + P\bar{Q}}$$