

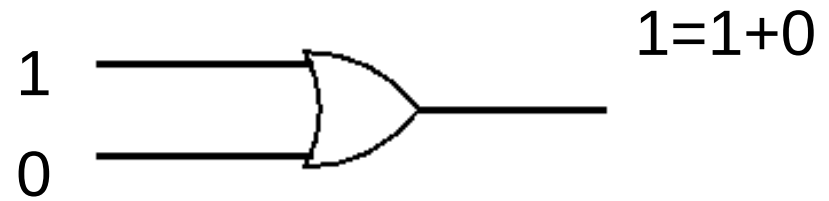
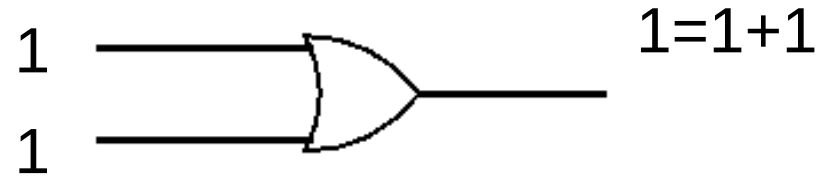
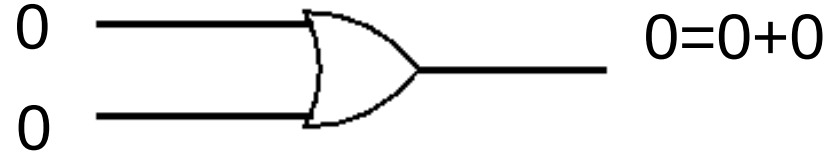
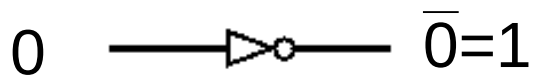
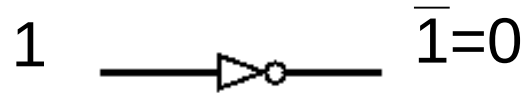
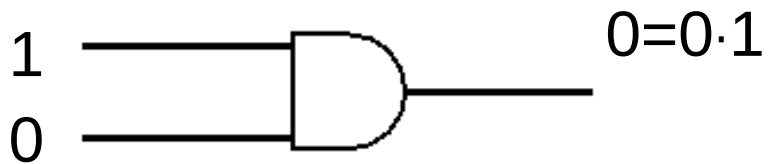


Postulates for AND – OR – NOT

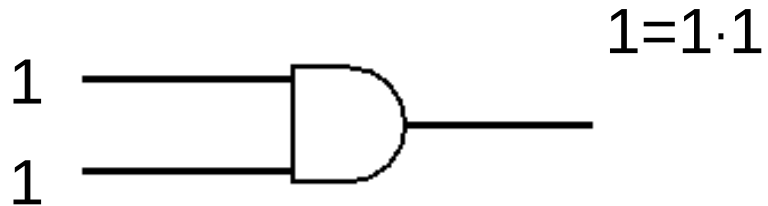
Postulates are self evident truths, facts



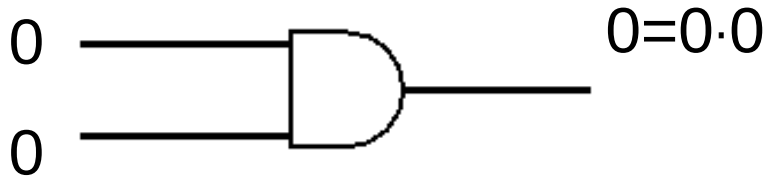

$0 \cdot 0 = 0$	$0 + 0 = 0$
$1 \cdot 1 = 1$	$1 + 1 = 1$
$1 \cdot 0 = 0$	$0 + 1 = 1$
$\bar{0} = 1$	$\bar{1} = 0$


Postulates for XOR – XNOR


Postulates are self evident truths, facts


0 0  0 = 0 ⊕ 0

1 1  0 = 1 ⊕ 1

1 0  1 = 1 ⊕ 0

0 0  1 = $\overline{0 \oplus 0}$

1 1  1 = $\overline{1 \oplus 1}$

1 0  0 = $\overline{0 \oplus 1}$

$0 \oplus 0 = 0$	$\overline{0 \oplus 0} = 1$
$1 \oplus 1 = 0$	$\overline{1 \oplus 1} = 1$
$1 \oplus 0 = 1$	$\overline{0 \oplus 1} = 0$

Algebraic Properties

Algebraic properties that we are familiar with

Commutative Property of Addition	$A + B = B + A$
Commutative Property of Multiplication	$A \cdot B = B \cdot A$
Associative Property of Addition	$(A + B) + C = A + (B + C)$
Associative Property of Multiplication	$(A \cdot B) \cdot C = A \cdot (B \cdot C)$
Distributive Property of Addition and Multiplication	$A \cdot (B + C) = AB + AC$ $(A + B) \cdot C = AC + BC$
Reciprocal of Nonzero Number	$A \cdot (1/A) = 1$
Additive Inverse	$A + (-A) = 0$
Additive Identity	$A + 0 = 0 + A = A$
Multiplicative Identity	$A \cdot 1 = 1 \cdot A = A$






Boolean Algebra Properties

Ordinary algebraic properties also apply to Boolean algebra.
Some are unique to Boolean algebra.

AND	OR	XOR
Commutative		
$AB = BA$	$A + B = B + A$	$A \oplus B = B \oplus A$
Associative		
$A(BC) = AB(C)$	$A + (B + C) = (A + B) + C$	$(A \oplus B) \oplus C = A \oplus (B \oplus C)$
Distributive		
$A(B + C) = AB + AC$	$A + BC = (A + B)(A + C)$	$A(B \oplus C) = AB \oplus AC$ $(A \oplus B)(A \oplus C) = \bar{A} B C + A \bar{B} \bar{C}$



Let us examine the Boolean algebra identities using logic gates

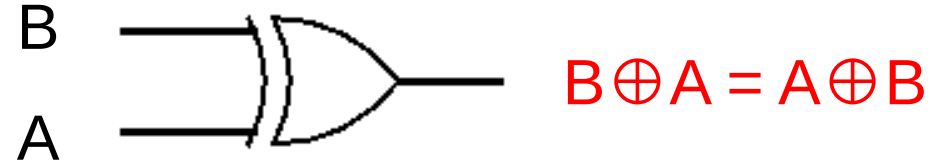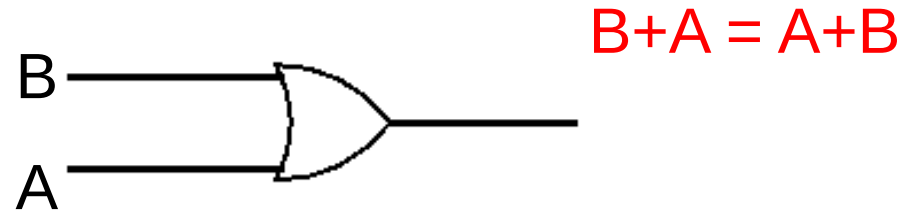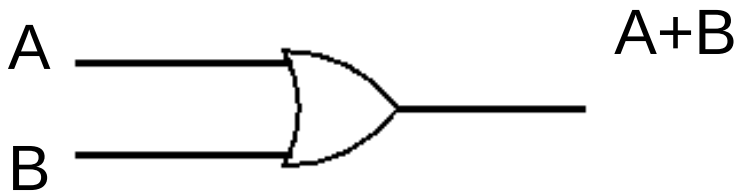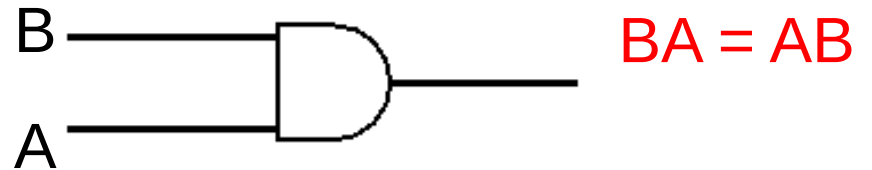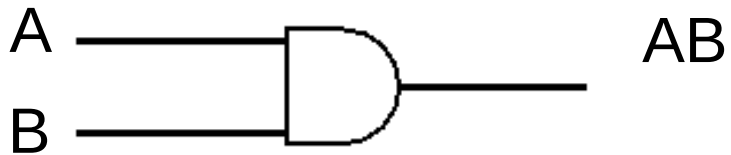Commutative Properties – Circuit Diagrams





Commutative property implies the circuit is not affected by the order or sequence of the variables (inputs)

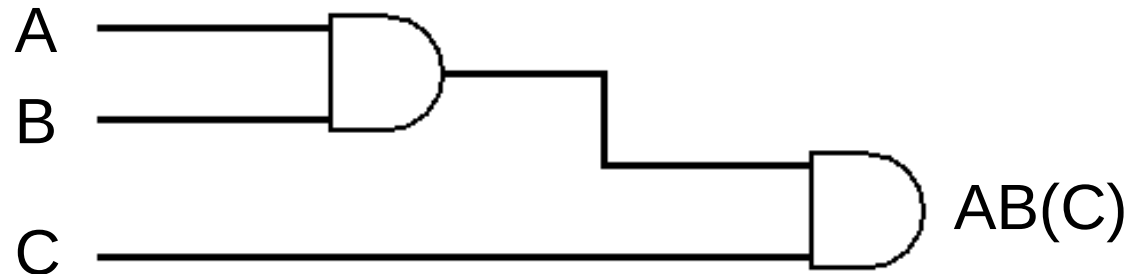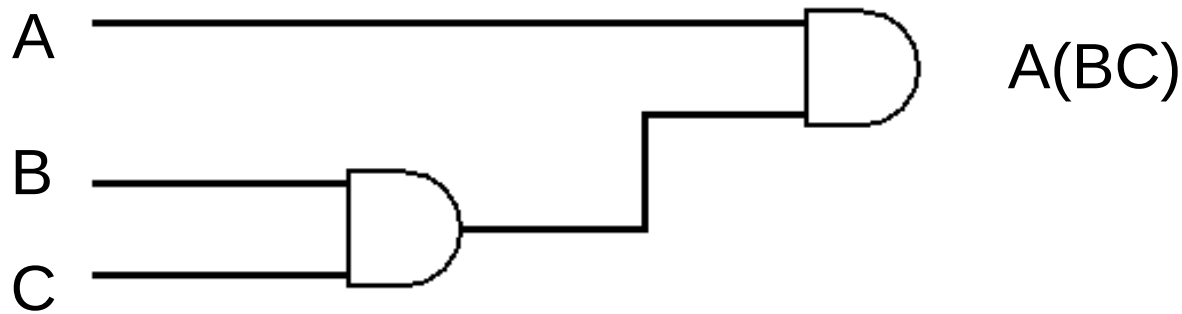Associative Properties for AND – Circuit Diagrams



Associative property implies that a sequence exclusively of AND functions is not affected by the placement of the parentheses.... $A(BC) = AB(C)$

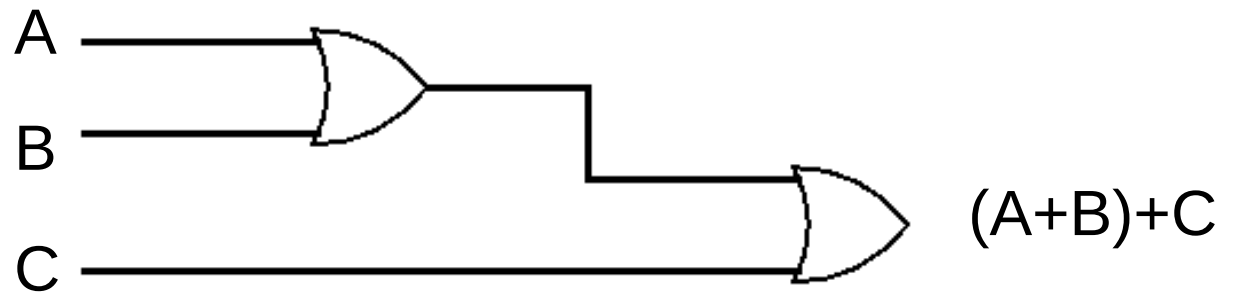
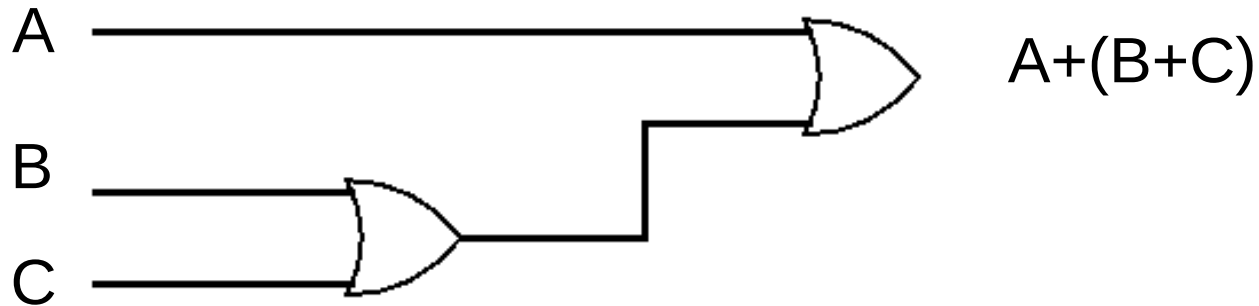
Associative Properties for OR – Circuit Diagrams



Associative property implies that a sequence exclusively of OR functions is not affected by the placement of the parentheses....

$$A+(B+C) = (A+B)+C$$

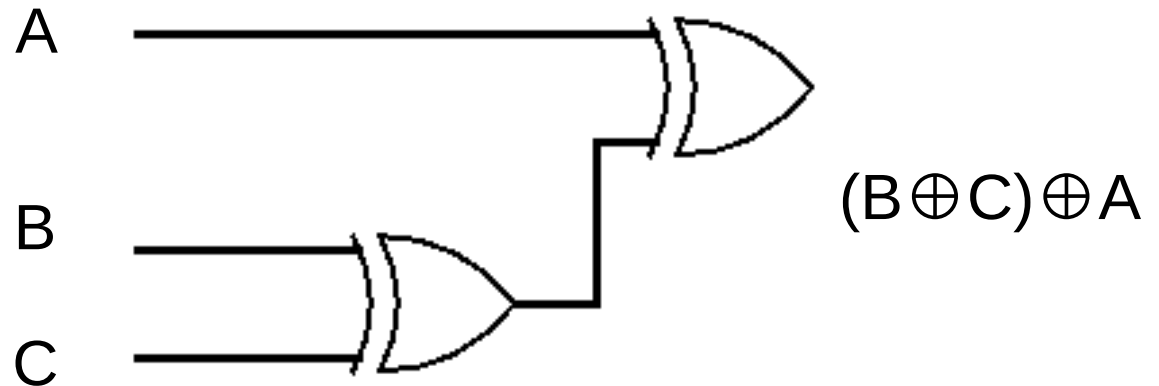
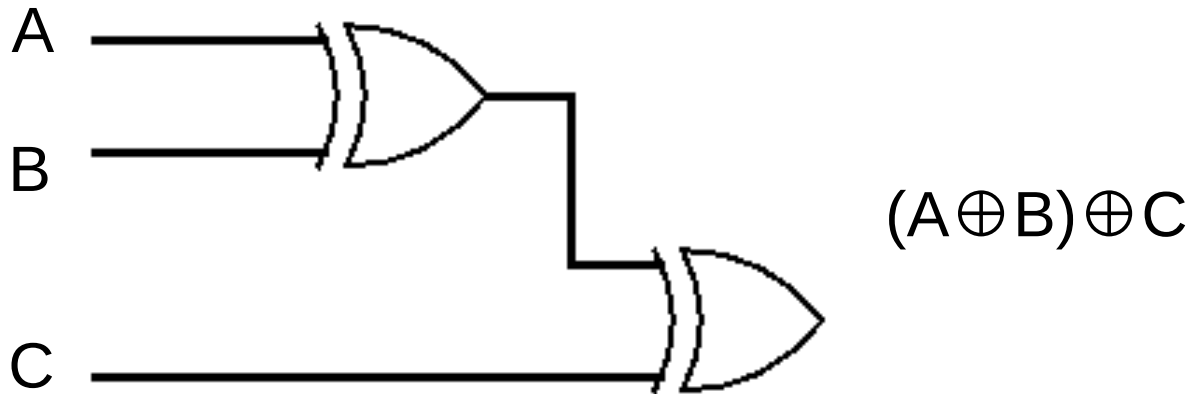
Associative Properties for XOR – Circuit Diagrams



Associative property implies that a sequence exclusively of OR functions is not affected by the placement of the parentheses....



$$(A \oplus B) \oplus C = (B \oplus C) \oplus A$$

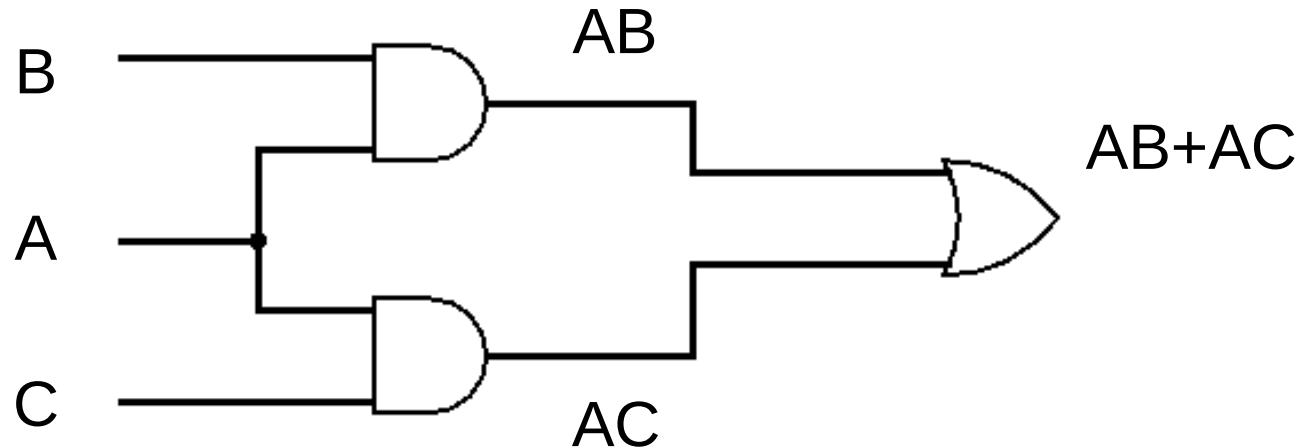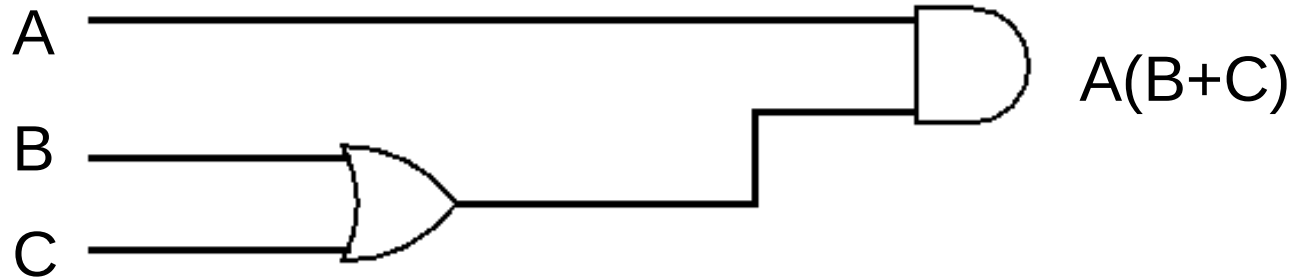Distributive Properties for AND/OR – Circuit Diagrams





Distributive property produces 2 forms of an expression...2 possible circuits.... $A(B+C) = AB+AC$

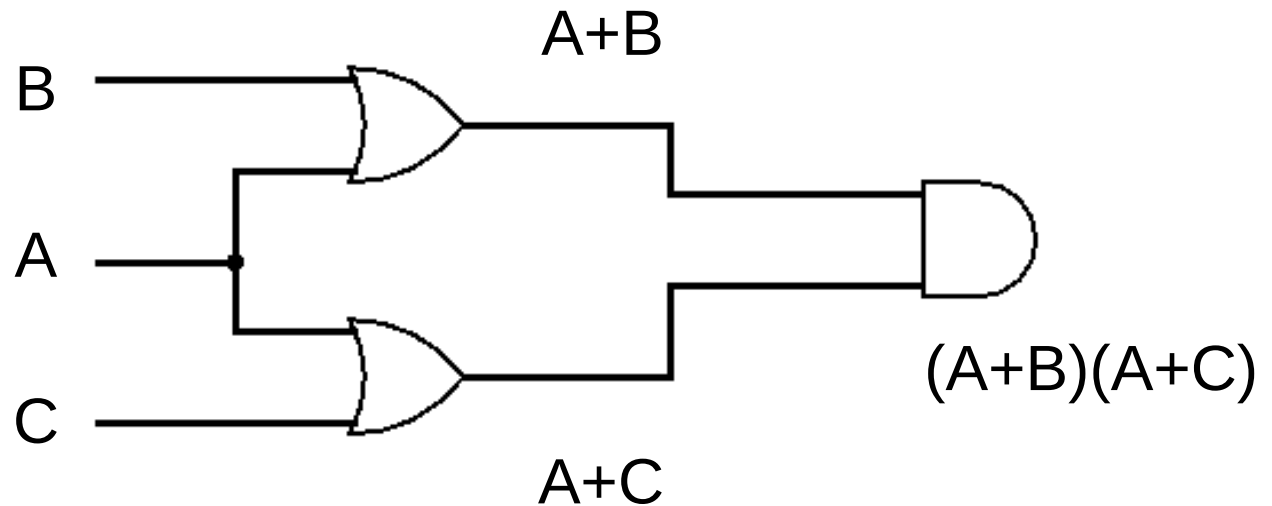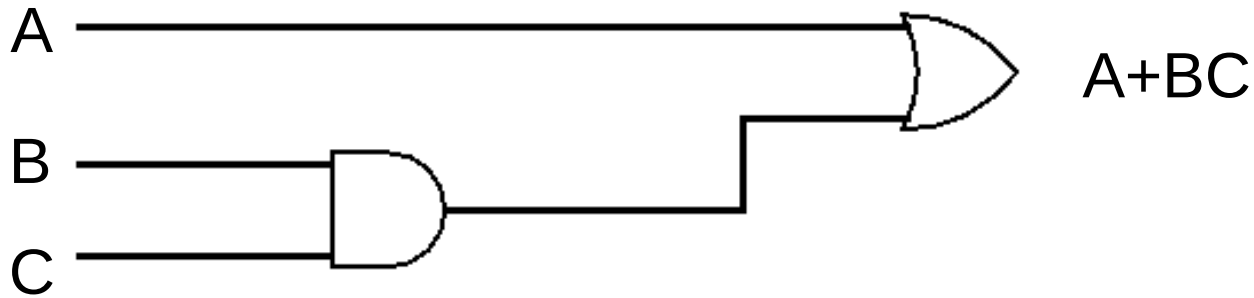Distributive Properties for AND/OR – Circuit Diagrams





Distributive property produces 2 forms of an expression...2 possible circuits.... $A+BC=(A+B)(A+C)$

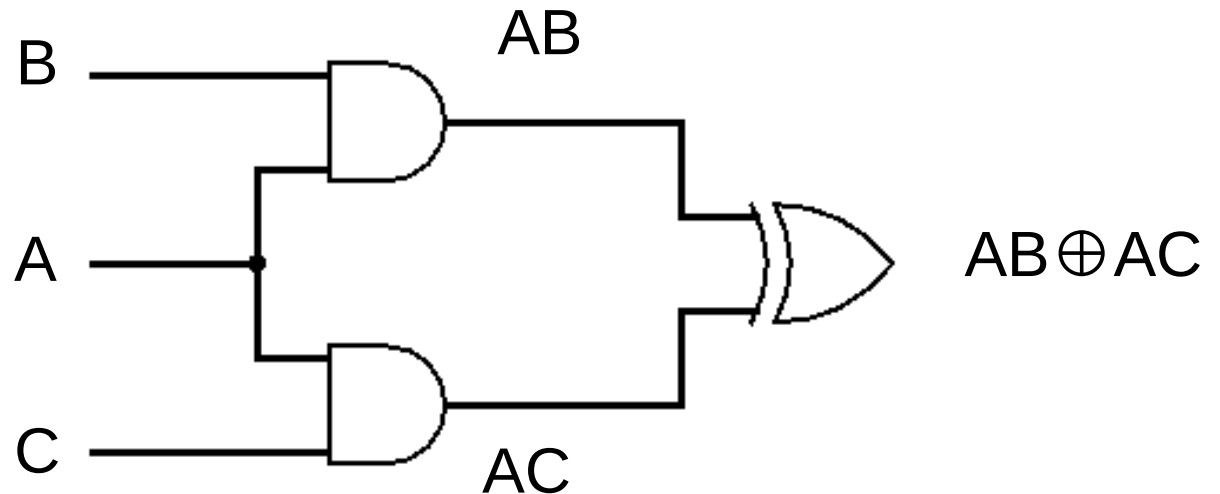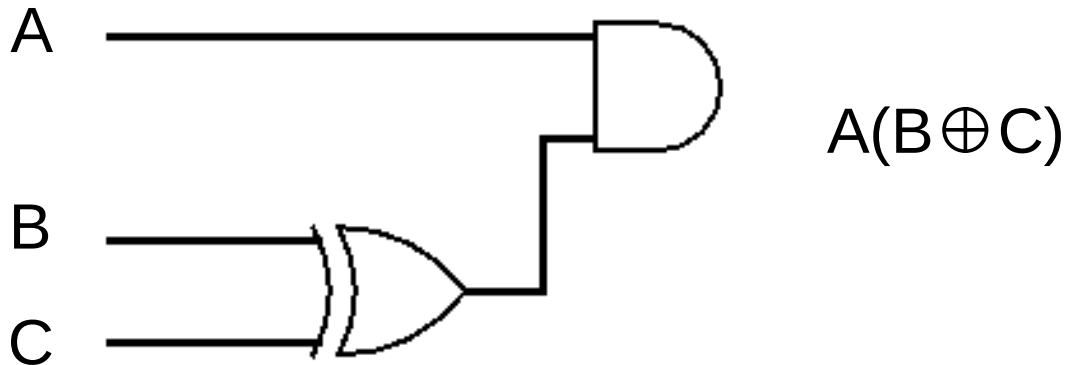Distributive Properties for XOR – Circuit Diagrams



Distributive property produces 2 forms of an expression...2 possible circuits.... $A(B \oplus C) = AB \oplus AC$

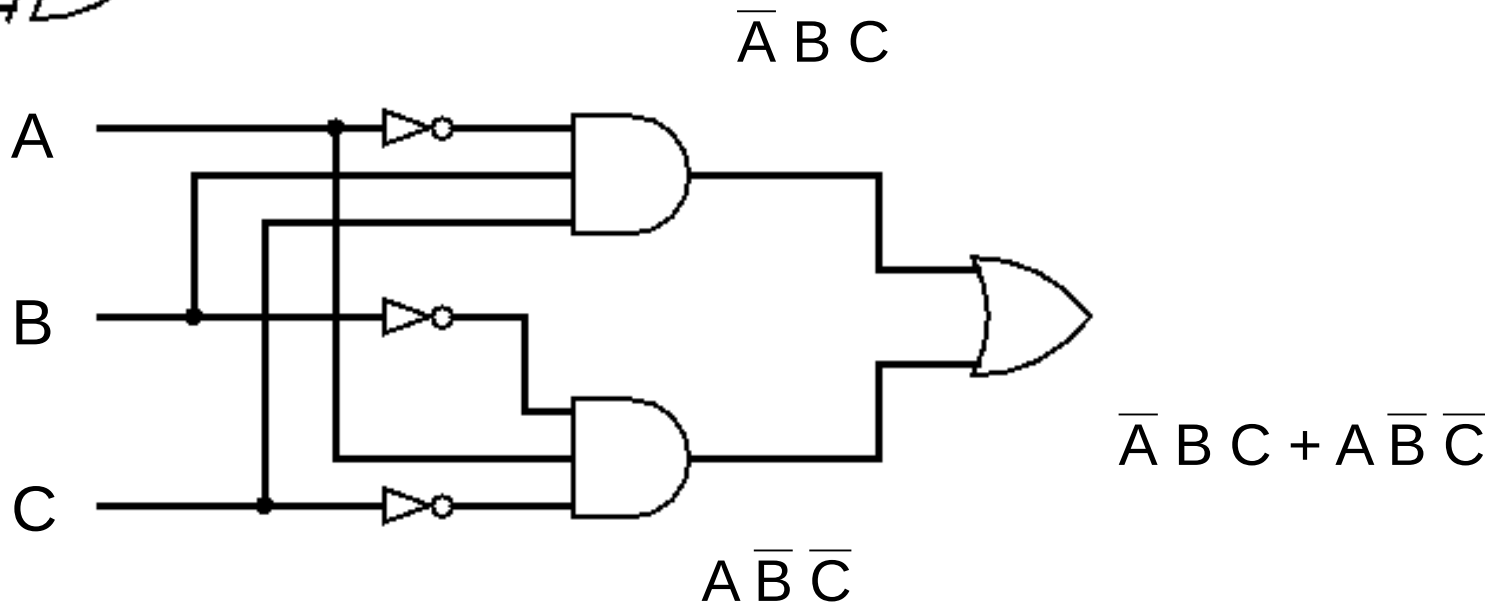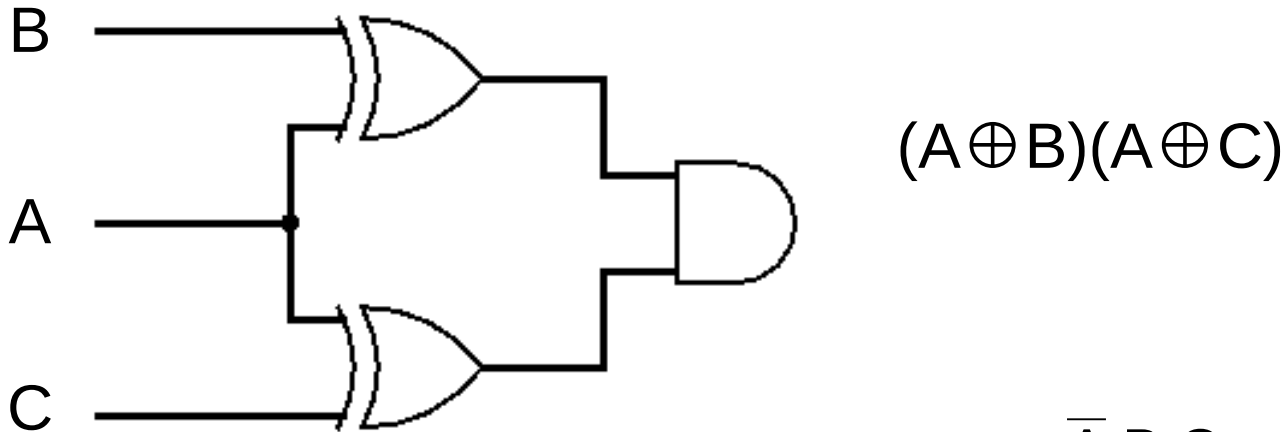Distributive Properties for XOR – Circuit Diagrams



Distributive property produces 2 forms of an expression...2 possible circuits.... $(A \oplus B)(A \oplus C) = \bar{A} B C + A \bar{B} \bar{C}$